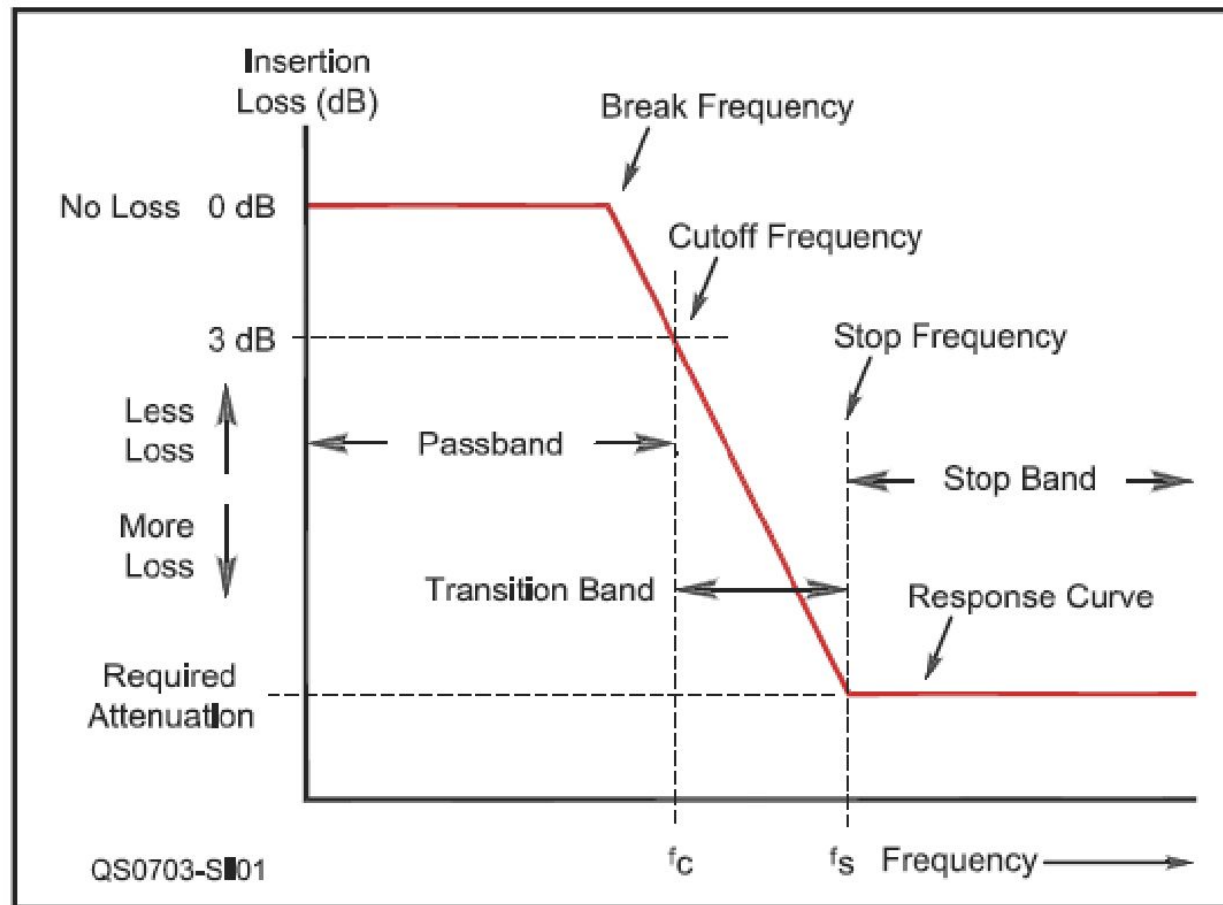




# Low Pass Filter Design Example & Simulation

1. Election
2. Treasury Duty Relief & Appointment
3. Any other business



## Example LPF Design

*Clean up a second harmonic at least 17dB below  $F_c$   
 $F_{reg} = 7 \text{ Mhz}$  and use a Butterworth filter. Shunt Type.*

*Impedance = 50 Ohm in and 50 Ohm out.*

*$F_c = 7 \text{ Mhz}$*


*$F_s = 14 \text{ Mhz}$*

*Normalised Freq. =  $F/F_c = 2.0$*

*Check Table for Frequency Response.*

*It shows  $N=4$*

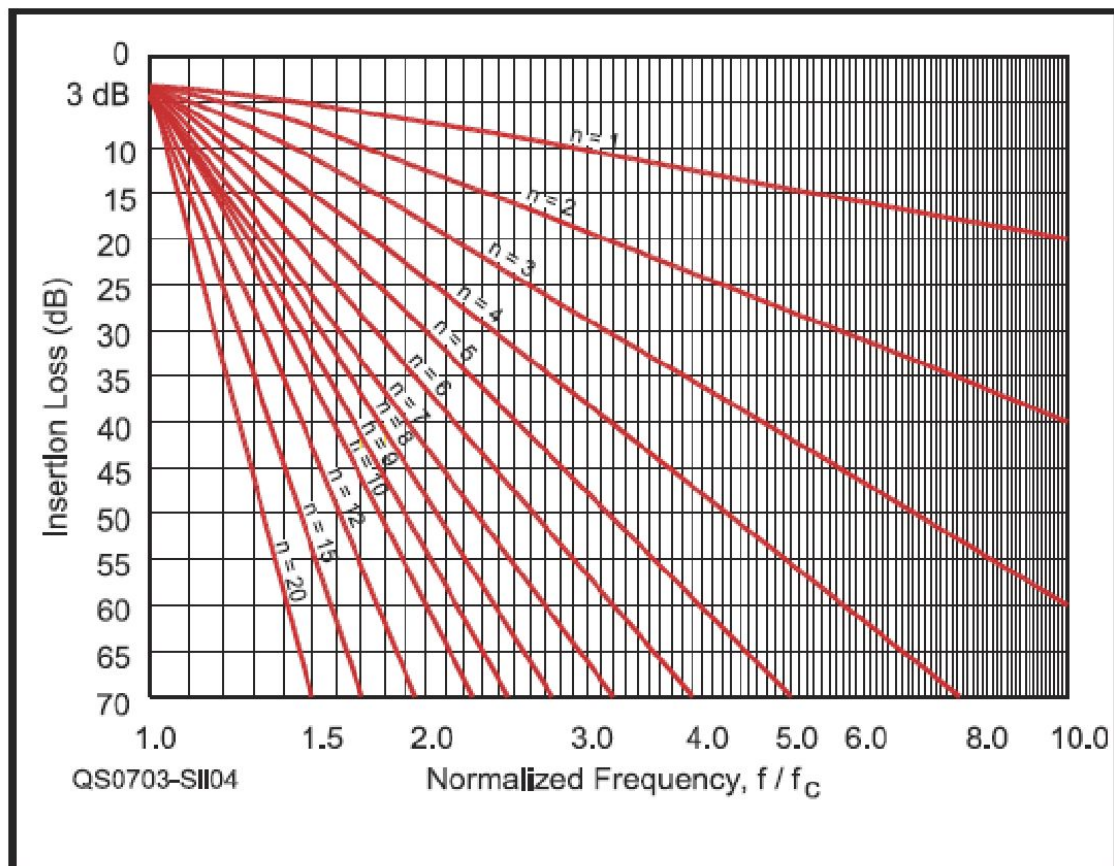*Check table with normalized  $L$  &  $C$  values*



# Prototype Butterworth Low-Pass Filters

	C1	L2	C3	L4	C5	L6
	L1	C2	L3	C4	L5	C6
n						
1	2.0000					
2	1.4142	1.4142				
3	1.0000	2.0000	1.0000			
4	0.7654	1.8478	1.8478	0.7654		
5	0.6180	1.6180	2.0000	1.6180	0.6180	
6	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470
8	0.3902	1.1111	1.6629	1.9616	1.9616	1.6629
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754


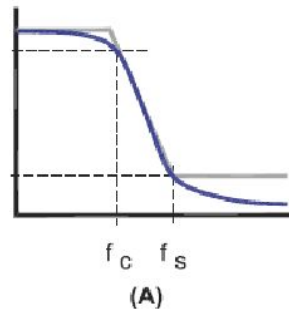
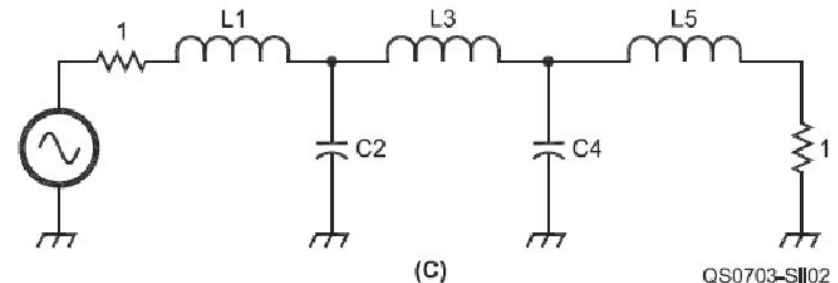


Figure 2 —

A — Table of normalized component values for a filter with a given number of poles, n.

B — The shunt-input filter schematic.

C — The series-input filter.

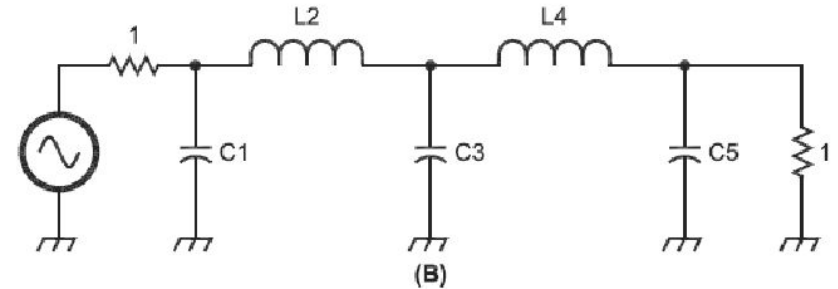


QS0703-SII02

## Example

*Check table with normalized L & C values*

$$C1 = 0.7654 \quad L2 = 1.8478$$

$$C3 = 1.8478 \quad L4 = 0.7654$$

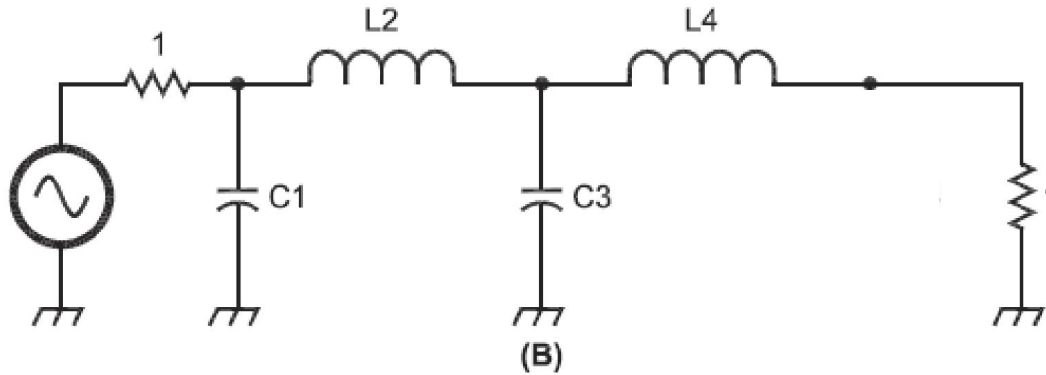

## Example work out

$$L2 = L * \left(\frac{50}{1}\right) * (1/(2\pi * Fc)) \text{ in Henry}$$

$$L2 = 1.8478 * \left(\frac{50}{1}\right) * (1/(2\pi * 7\text{Mhz})) \text{ in Henry}$$

$$L2 = 2.1\mu H$$

$$C1 = C * (1/50) * (1/(2\pi * Fc)) \text{ in Farad}$$


$$C1 = 0.7654 * (1/50) * (1/(2\pi * 7\text{Mhz})) \text{ in Farad}$$

$$C1 = 348\text{pF}$$

Same Process:

$$C3 = 840\text{pF}$$


$$L4 = 870\text{nH or } 0.87\mu H$$

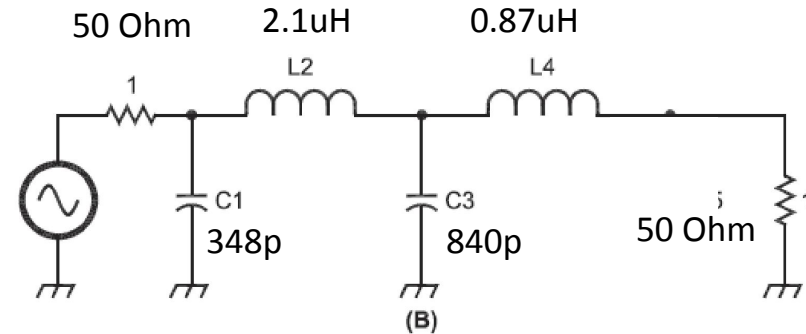




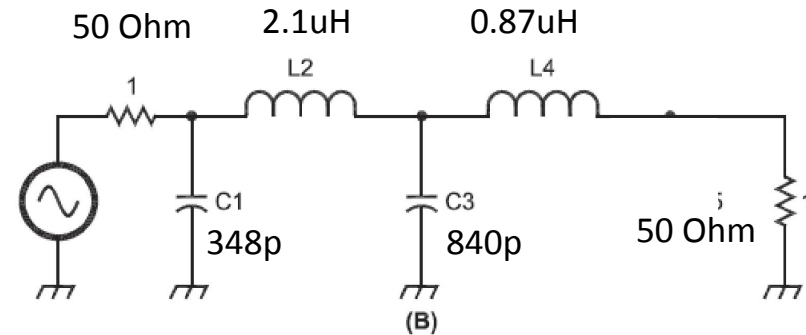
## Things to Consider


- Insertion loss and Amplification
- Standard Values versus Calc values
- Coil Type.
- Do you like a high or low Q
- C suitability for the target Frequency
- C max Voltage
- L max Current or Power Rating
- L and T dependence.
- Keep in mind tolerances of C & L
- Rp for C
- Rs for L
- Humidity impact
- T impact on permanent change of C
- G forces impact / Mechanical Structure
- Ultimate Rejection



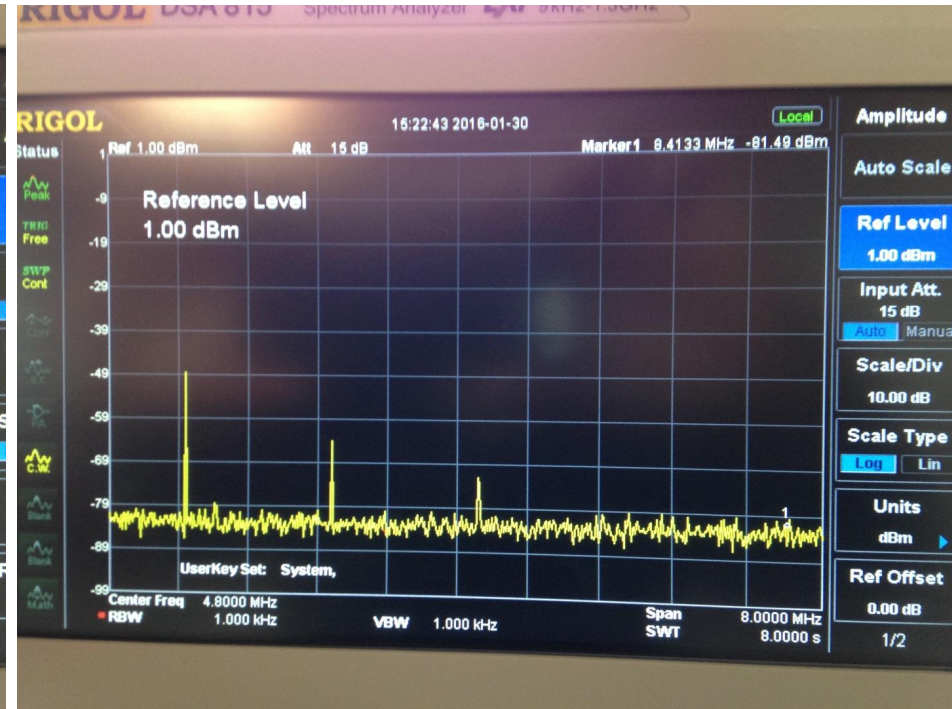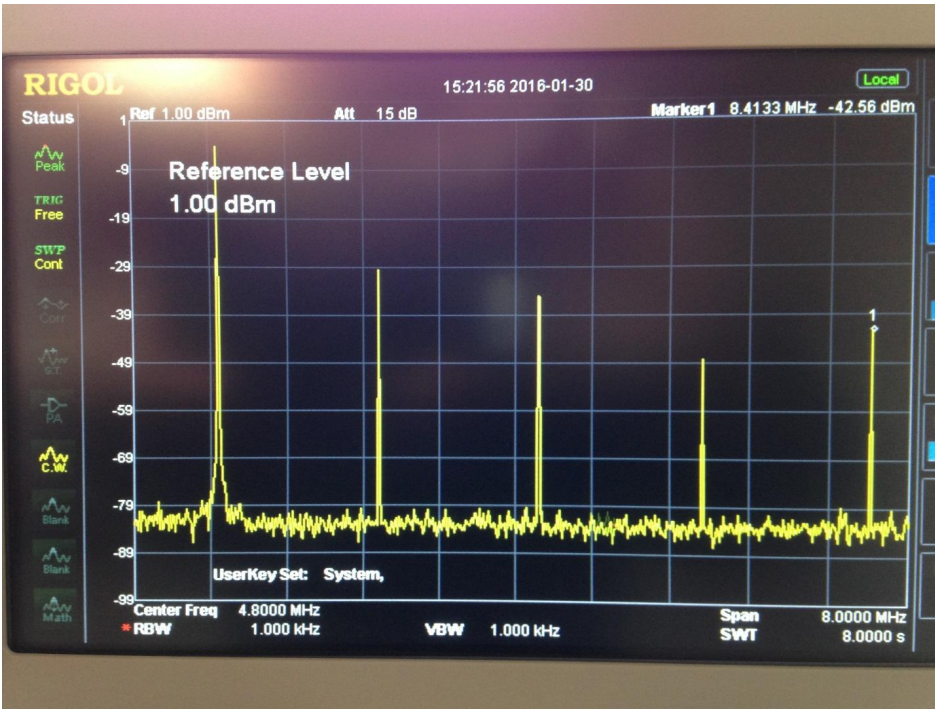
Too much attenuation 5<sup>th</sup> order LPF  
Example of 1680kHz Low Power Transmitter ( 10mW).  
Left no filter / Right after filter .



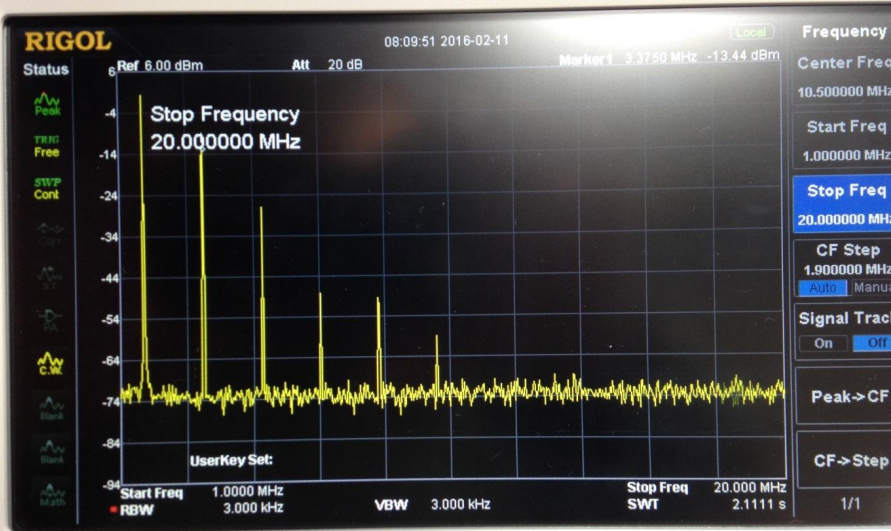Before and After . Improved matching but still too much attenuation 5<sup>th</sup> order  
LPF  
Output becomes micro watt QRP levels.




TIARA FEBRUARY 19 2016

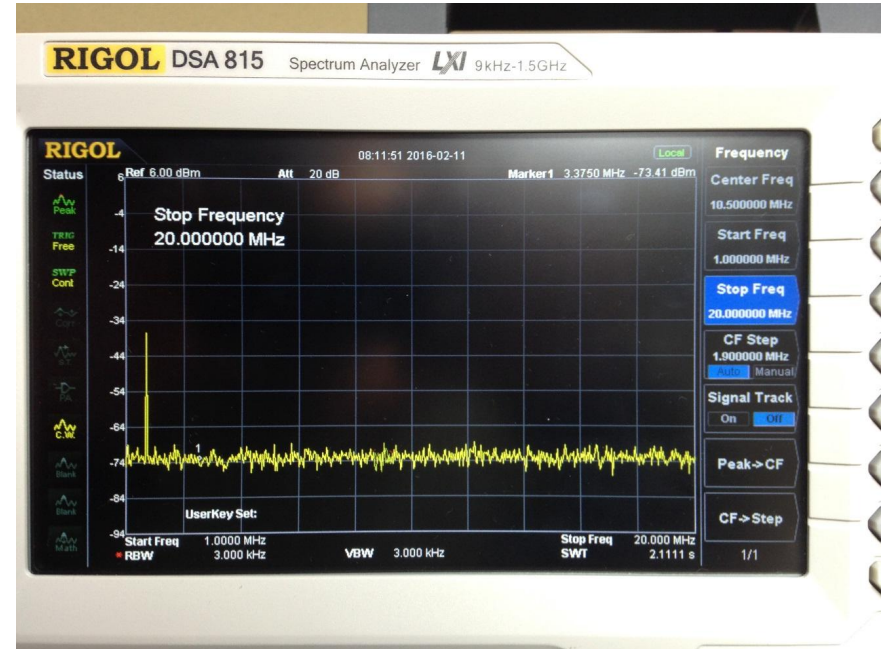

ARIE LUKKASSEN



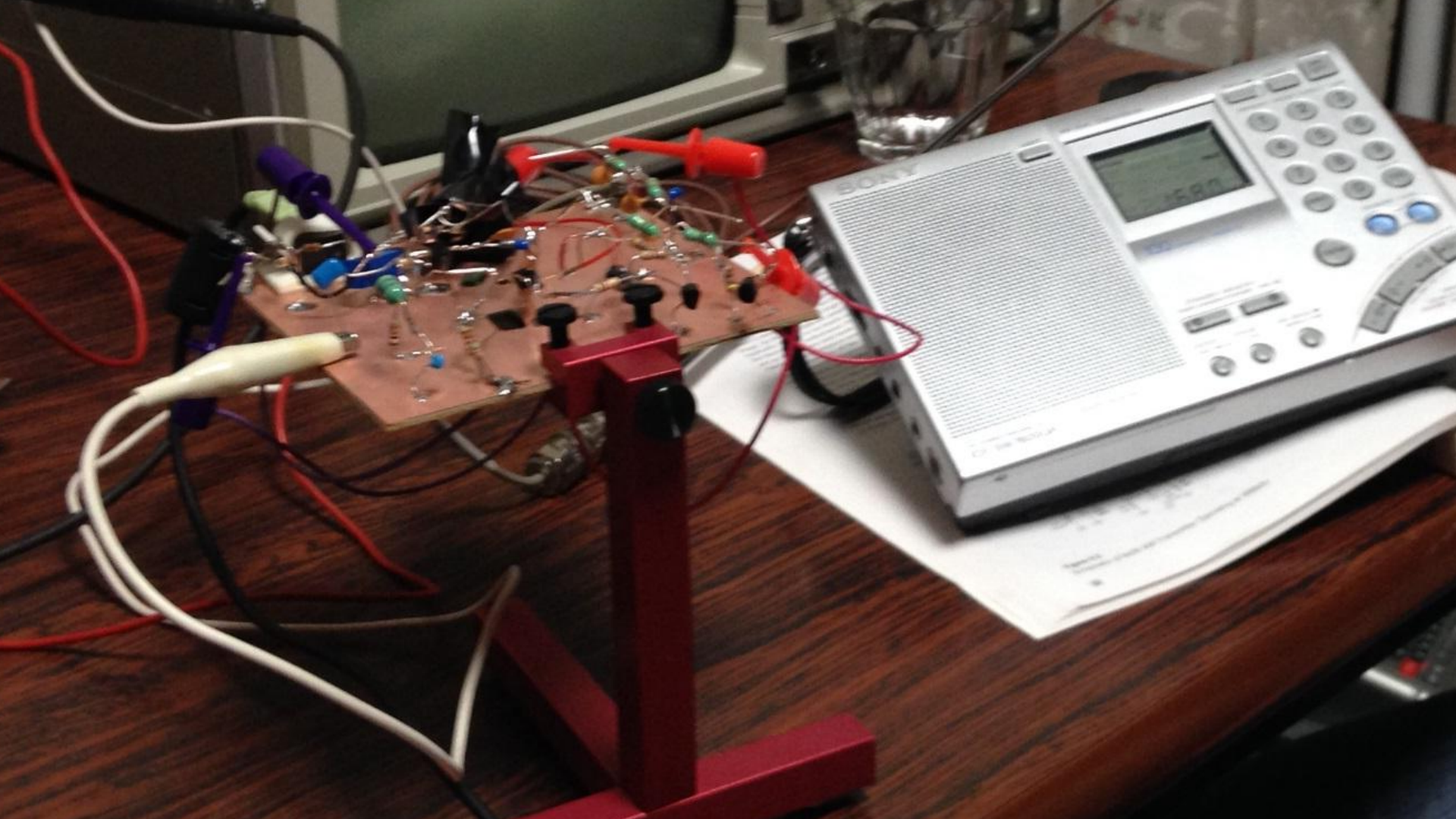

# Sources and References: ARRL 2006 Handbook

NOW  
SIMULATION  
Tina Simulator  
TI Student Version